

UNIVERSITY OF SOUTHERN CALIFORNIA

USC VITERBI SCHOOL OF ENGINEERING

MING HSIEH DEPARTMENT OF ELECTRICAL ENGINEERING

EE 348: FINAL EXAMINATION #3
(OPEN NOTES, HOMEWORK)

MAY 08, 2007
11:00-TO-1:00

PROBLEM #1:

(45%)

Except for possible differences in gate aspect ratios, all transistors in the two-stage differential amplifier of Figure (E1) are identical. All transistors are biased in saturation, have infinitely large channel resistances, and boast negligible bulk-induced threshold voltage modulation. The capacitances, C and C_p , are sufficiently large to enable them to function as respective short circuits for the signal frequencies of interest.

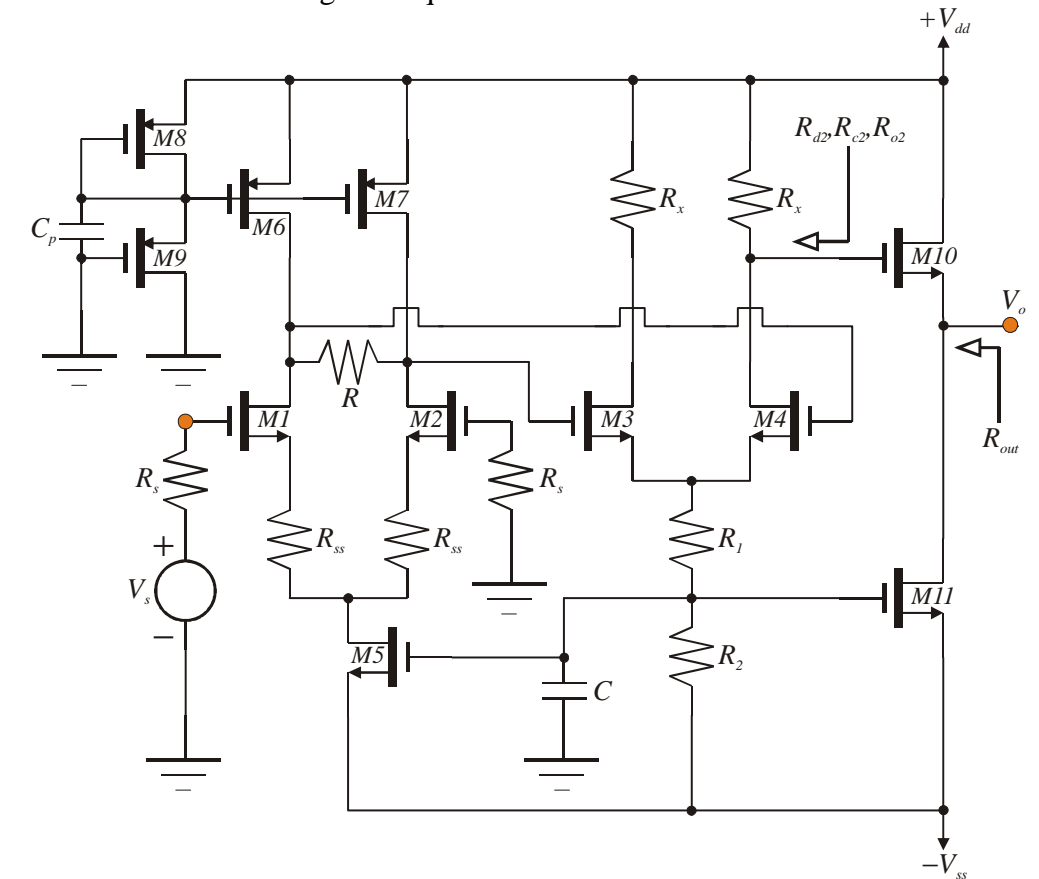



Fig. (E1)

- (a). Respond to the following queries as briefly and as clearly as you can.
- (a1). Under small signal operating conditions, what fundamental purpose is served by the current sink formed of transistor $M5$ and its associated biasing?
 - (a2). Note that the second differential stage comprised of transistors $M3$ and $M4$ does not use active current sinking at the source terminal interconnection of these devices. Why might active current sinking here be construed as unnecessary?
 - (a3). What purpose is served by the indicated interconnection of transistors $M8$ and $M9$?

- (a4). What purposes are served by capacitances C and C_p ?
- (a5). Is the circuit a balanced architecture? If it is not balanced, what electrical connection must be severed to establish balance?
- (b). Under balanced conditions and in terms of input voltage signal V_s and appropriate transistor and circuit parameters, determine the differential signal voltage, say V_{di2} , established from the gate of transistor $M3$ to the gate of transistor $M4$.
- (c). Under balanced conditions and in terms of input voltage signal V_s and appropriate transistor and circuit parameters, determine the common mode signal voltage, say V_{ci2} , established with respect to signal ground at the individual gates of transistors $M3$ and $M4$.
- (d). Give expressions for the differential mode, the common mode, and actual output resistances, R_{d2} , R_{c2} , and R_{o2} , respectively, “seen” by the gate of transistor $M10$.
- (e). Give an expression for the small signal voltage gain, $A_v = V_{os}/V_s$.
- (f). What is the output resistance, R_{out} ?

PROBLEM #2:**(40%)**

In the current amplifier shown in Figure (E2), the input signal is the signal component, I_s , to the net input current, $I_Q + I_s$, while the output response to the signal input is taken as the signal component, I_{Ls} , to the indicated current, $I_{LQ} + I_{Ls}$. Of course, I_{LQ} and I_Q are quiescent biasing currents. Transistors $M1$ and $M2$ are identical, save for the fact that the gate aspect ratio of transistor $M1$ is *k-times smaller* than the gate aspect ratios of transistors $M2$ and $M3$. All transistors are biased in saturation, have infinitely large channel resistances, and have negligibly small bulk-induced threshold modulation.

 **Fig. (E2)**

- (a). Under quiescent operating conditions, express in terms of the aspect ratio parameter, k , the relationship among the device transconductances, g_{m1} , g_{m2} , and g_{m3} .
- (b). Draw the low frequency, small signal equivalent circuit of the network.
- (c). Derive an expression for the small signal, low frequency input resistance, R_{in} . Express your result in terms of appropriate circuit parameters and device transconductances.
- (d). Derive an expression for the low frequency, small signal current gain, $A_i = I_{Ls}/I_s$. Simplify your result for the case of very large R and express the result in terms of parameter k .
- (e). Derive an expression for the 3-dB bandwidth, B , of this current gain. Assume that all capacitances indigenous to the three transistors are negligibly small.
- (f). If the resistances, R and R_L , satisfy the inequality, $R > kR_L$, briefly discuss any problems encountered with respect to sustaining the operation of transistor $M3$ in saturation.

PROBLEM #3:**(15%)**

Return to the circuit in Figure (E1).

- (a). Let transistors $M8$ and $M9$ be identical, inclusive of gate aspect ratios. If transistors $M6$ and $M7$ are biased so that their respective source to drain quiescent voltages are one P-channel threshold voltage above their source-drain saturation voltage, what quiescent voltage is established with respect to ground at the drains of transistors $M1$ and $M2$?
 - (b). Let the quiescent voltage developed with respect to ground at the drain of transistor $M5$ be V_Q and let this same static voltage prevail at the source interconnection of transistors $M3$ and $M4$. Will transistor $M5$ operate in saturation for any values of resistances R_1 and R_2 ?
 - (c). What detrimental impact on the small signal performance of the amplifier is likely to be observed if transistor $M5$ operates in its triode domain?
 - (d). How much power is dissipated by resistance R under quiescent operating conditions?
 - (e). For differential mode small signal operation, how must capacitance C be chosen so that C emulates a short circuit for all signal frequencies above ω_L ?
 - (f). For differential mode small signal operation, how must capacitance C_p be chosen so that C_p emulates a short circuit for all signal frequencies above ω_L ?
-
-